

Sistemas Digitais

Aprendendo VHDL por Exemplos

Embedded System Design – Vahid e Givargis

Logic and Computer Design Fundamentals – M. Mano e C. Kime

FPGA Prototyping by VHDL Examples – Pong P. Chu

VHDL para Porta AND


Descrição Comportamental

```
-- AND gate (ESD book figure 2.3) |
```

```
library ieee;  
use ieee.std_logic_1164.all;
```

```
entity AND_ent is  
port(  
  x: in std_logic;  
  y: in std_logic;  
  F: out std_logic  
);  
end AND_ent;
```
 
```
architecture behav2 of AND_ent is  
begin  
  
  F <= x and y;  
  
end behav2;
```



$F = x \cdot y$
AND

x	y	F
0	0	0
0	1	0
1	0	0
1	1	1

- Para colocar comentários num arquivo VHDL, basta iniciar a linha com dois traços (--)
- Um comentário se estende desde os dois traços (--) até o fim da linha
- A *entity* define as entradas e saídas do circuito
- A *architecture* define o que o circuito faz

VHDL para Porta NOR


Descrição Comportamental

```
-- NOR gate (ESD figure 2.3)|
```

```
library ieee;  
use ieee.std_logic_1164.all;
```

```
entity NOR_ent is  
port(  
    x: in std_logic;  
    y: in std_logic;  
    F: out std_logic  
);  
end NOR_ent;
```
 
```
architecture behv2 of NOR_ent is  
begin  
  
    F <= x nor y;  
  
end behv2;
```



A *library* faz com que uma determinada biblioteca (neste caso **ieee**) seja carregada na compilação atual

O *use* delimita quais itens da biblioteca devem estar visíveis para a subsequente unidade de projeto (*entity* + *architecture*)

VHDL para Porta Driver


Descrição Comportamental

```
-----  
-- driver (ESD book figure 2.3)  
-----
```

```
library ieee;  
use ieee.std_logic_1164.all;
```

```
-----  
entity Driver is  
port(   x: in std_logic;  
       F: out std_logic  
);  
end Driver;
```
 
```
-----  
architecture behv2 of Driver is  
begin  
  
    F <= x;  
  
end behv2;
```



x	F
0	0
1	1

$F = x$
Driver

VHDL para Porta XNOR


Descrição Comportamental

```
-- XOR gate (ESD figure 2.3)
```

```
library ieee;  
use ieee.std_logic_1164.all;
```

```
entity XNOR_ent is  
port(  
    x: in std_logic;  
    y: in std_logic;  
    F: out std_logic  
);  
end XNOR_ent;
```
 
```
architecture behv2 of XNOR_ent is  
begin  
  
    F <= x xnor y;  
  
end behv2;
```



$F = x \odot y$
XNOR

x	y	F
0	0	1
0	1	0
1	0	0
1	1	1

Como XNOR é uma palavra reservada do VHDL, ela não pode ser usada como nome de uma entidade ou arquitetura (por isso foi escolhido XNOR_ent)

VHDL para Porta NAND

Descrição Comportamental

```
-- NAND gate (ESD figure 2.3)
-----

library ieee;
use ieee.std_logic_1164.all;

-----

entity NAND_ent is
port(   x: in std_logic;
       y: in std_logic;
       F: out std_logic
);
end NAND_ent;

-----

architecture behv1 of NAND_ent is
begin

    process(x, y)
    begin
        if (x='1' and y='1') then
            F <= '0';
        else
            F <= '1';
        end if;
    end process;


end behv1;

-----

architecture behv2 of NAND_ent is
begin

    F <= x nand y;

end behv2;
```

 

$F = (x y)'$
NAND

x	y	F
0	0	1
0	1	1
1	0	1
1	1	0

Uma *entity* pode ter mais de uma *architecture* associada a ela, mas durante a simulação apenas uma delas estará ativa

A decisão será feita pelo simulador baseada numa declaração no final do arquivo, chamada *configuration* (ou na ausência de uma *configuration* será utilizada a última *architecture* compilada)

Exemplo de Comparador de 1 Bit

entrada **saída**

i0i1 *eq*


00 1

01 0

10 0

11 1

$$eq = i0.i1 + i0 \bar{i1}$$

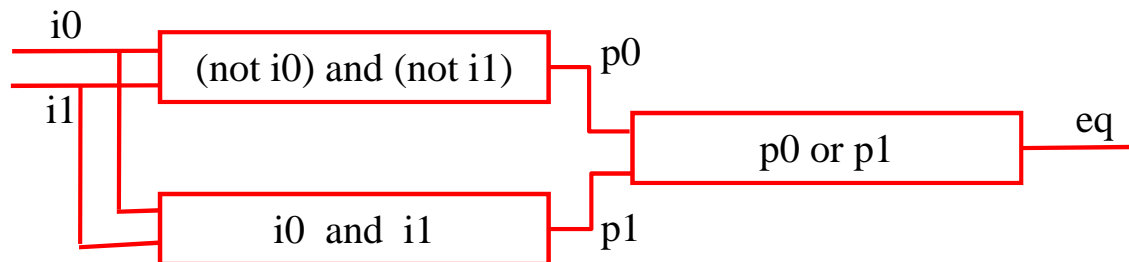

-- Listing 1.1

library ieee;

use ieee.std_logic_1164.all;

entity eq1 **is**

port(

 i0, i1: **in** std_logic;

 eq: **out** std_logic

);

end eq1;

architecture sop_arch **of** eq1 **is**

signal p0, p1: std_logic;

begin

 -- sum of two product terms

 eq <= p0 or p1;

 -- product terms

 p0 <= (**not** i0) **and** (**not** i1);

 p1 <= i0 **and** i1;

end sop_arch;

Testbench para o Comparador de 1 Bit

-- Listing 1.1b - Testbench (adaptação)

```
library ieee;
```

```
use ieee.std_logic_1164.all;
```

```
entity eq1_testbench is
```

```
end eq1_testbench;
```

```
architecture tb_arch of eq1_testbench is
```

```
    signal test_in0, test_in1: std_logic;
```

```
    signal test_out: std_logic;
```

```
begin
```

```
    -- instancia o circuito sob test (uut - unit under test)
```

```
    uut: entity work.eq1(sop_arch)
```

```
        port map(i0=>test_in0, i1=>test_in1, eq=>test_out);
```

```
    -- gerador dos vetores de teste
```

```
process
```


```
begin
```

```
    -- vetor de teste 1
```

```
    test_in0 <= '0';
```

```
    test_in1 <= '0';
```

```
    wait for 200 ns;
```

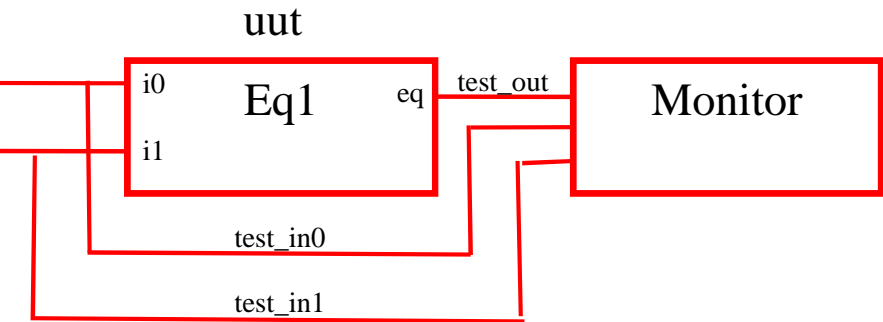

```
-- vetor de teste 2
```

```
test_in0 <= '0';
```

```
test_in1 <= '1';
```

```
wait for 200 ns;
```

```
-- vetor de teste 3
```

```
test_in0 <= '1';
```

```
test_in1 <= '0';
```

```
wait for 200 ns;
```

```
-- vetor de teste 4
```

```
test_in0 <= '1';
```

```
test_in1 <= '1';
```

```
wait for 200 ns;
```

```
wait;
```

```
end process;
```

```
end tb_arch;
```

Um *testbench* é usado para produzir os sinais de teste de um dispositivo modelado em VHDL

Processo em VHDL

- Um processo em VHDL é usado nas descrições comportamentais (*behavioral*)
- Exemplo simples de processo em VHDL:

```
ARCHITECTURE behavioral OF clock_component IS
BEGIN
  PROCESS
    VARIABLE periodic: BIT := '1';
    BEGIN
      IF en = '1' THEN
        periodic := not periodic;
      END IF;
      ck <= periodic;
      WAIT FOR 1 us;
    END PROCESS;
END behavioral;
```

Sintaxe de um Processo

```
[ process_label : ] PROCESS
[ ( sensitivity_list ) ]
    process_declarations
BEGIN
    process_statements
END PROCESS [ process_label ] ;
```

Nenhuma
DECLARAÇÃO de SIGNAL
dentro de um Processo!




Um Modelo de VHDL ...




```
ENTITY full_adder IS  
    PORT ( A, B, Cin : IN BIT;  
          Sum, Cout : OUT BIT );  
END full_adder;
```

 É possível construir a Arquitetura de um Somador Completo (Full Adder) usando estas portas?



Arquitetura do Somador Completo (Full Adder)

A	B	Cin	Sum	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

 


for Cout (I.e. Carry Out):

A B	Cin (I.e. Carry In)	
	0	1
0 0	0	0
0 1	0	1
1 1	1	1
1 0	0	1

for Sum:

A B	Cin (I.e. Carry In)	
	0	1
0 0	0	1
0 1	1	0
1 1	0	1
1 0	1	0

Dois Processos para o *Full Adder*

 

```
Summation:  
PROCESS( A, B, Cin)  
BEGIN  
    Sum <= A XOR B XOR Cin;  
END PROCESS Summation;
```

```
Carry:  
PROCESS( A, B, Cin)  
BEGIN  
    Cout <= (A AND B) OR  
            (A AND Cin) OR  
            (B AND Cin);  
END PROCESS Carry;
```

Arquitetura Completa

```
ARCHITECTURE example OF full_adder IS
    -- Nothing needed in declarative block...
BEGIN

    Summation: PROCESS( A, B, Cin)
        BEGIN
            Sum <= A XOR B XOR Cin;
        END PROCESS Summation;

    Carry: PROCESS( A, B, Cin)
        BEGIN
            Cout <= (A AND B) OR
                    (A AND Cin) OR
                    (B AND Cin);
        END PROCESS Carry;

END example;
```

Processo Alternativo para o Carry (Cout)


```
Carry: PROCESS( A, B, Cin)
BEGIN
  IF ( A = '1' AND B = '1' ) THEN
    Cout <= '1';
  ELSIF ( A = '1' AND Cin = '1' ) THEN
    Cout <= '1';
  ELSIF ( B = '1' AND Cin = '1' ) THEN
    Cout <= '1';
  ELSE
    Cout <= '0';
  END IF;
END PROCESS Carry;
```

for Cout (I.e. Carry Out):


A B	Cin (I.e. Carry In)	
	0	1
00	0	0
01	0	1
11	1	1
10	0	1

Multiplexador

Exemplo 1 de Circuito Combinacional

 

Multiplexador 4 x 1

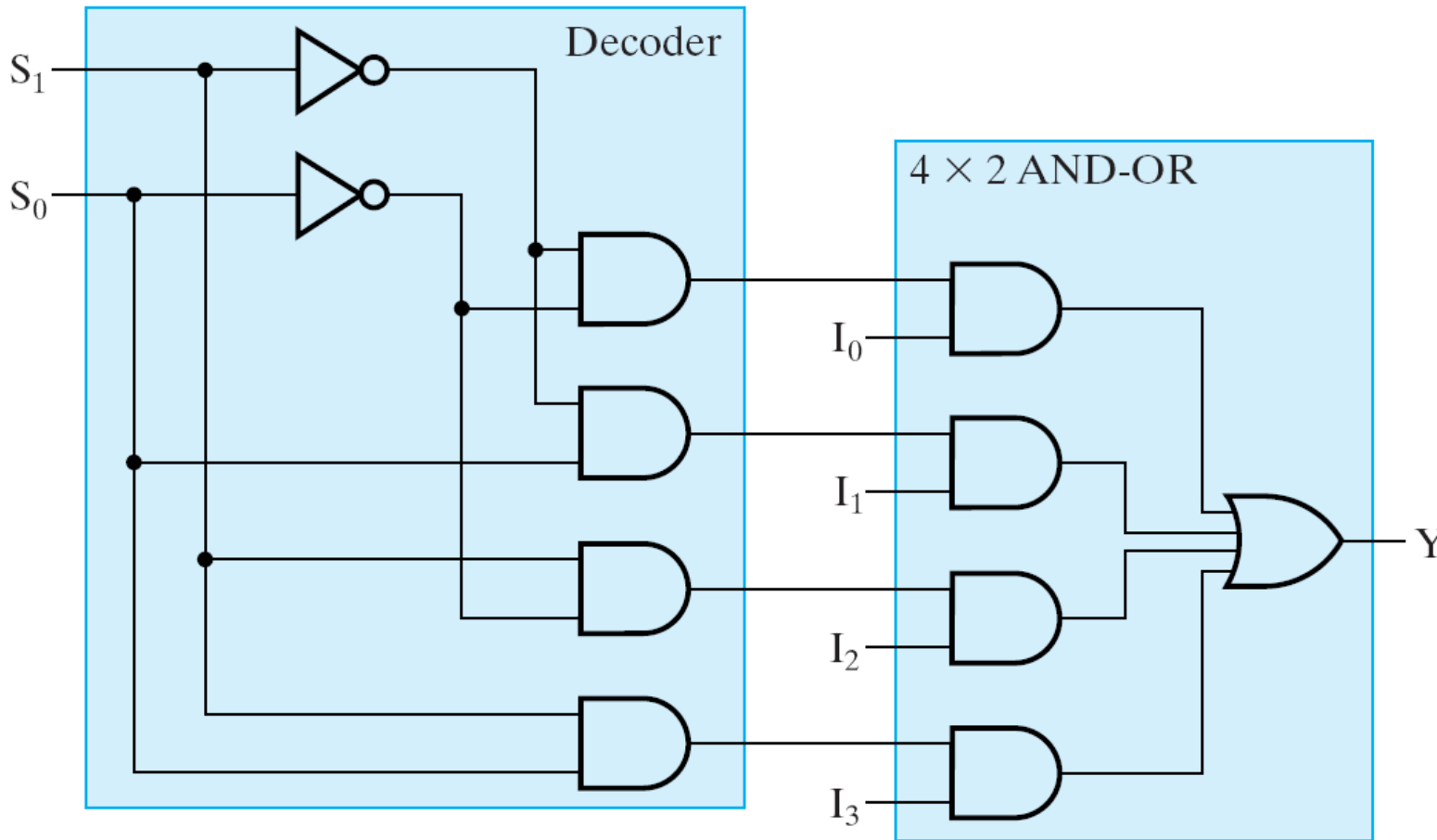

S_1	S_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

VHDL para Multiplexador 4 x 1

Descrição Fluxo de Dados

```
-- 4-to-1 Line Mux: Conditional Dataflow VHDL Description -- 1
-- Using When-Else (See Table 4-7 for function table) -- 2
library ieee; -- 3
use ieee.std_logic_1164.all; -- 4
entity multiplexer_4_to_1_we is -- 5
port (S : in std_logic_vector(1 downto 0); -- 6
      I : in std_logic_vector(3 downto 0); -- 7
      Y : out std_logic); -- 8
end multiplexer_4_to_1_we; -- 9
-- 10


architecture function_table of multiplexer_4_to_1_we is -- 11
begin -- 12
Y <= I(0) when S = "00" else -- 13
I(1) when S = "01" else -- 14
I(2) when S = "10" else -- 15
I(3) when S = "11" else -- 16
'X'; -- 17
end function_table; -- 18
```

S ₁	S ₀	Y
0	0	I ₀
0	1	I ₁
1	0	I ₂
1	1	I ₃

Decodificador 2 x 4

Exemplo 2 de Circuito Combinatório

EN	A₁	A₀	D₀	D₁	D₂	D₃
0	X	X	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1

 

VHDL para Decodificador 2 x 4


Descrição Fluxo de Dados

```
-- 2-to-4 Line Decoder: Dataflow VHDL Description
-- (See Figure 4-10 for logic diagram)
Use library, use, and entity entries from 2_to_4_decoder_st;

architecture dataflow_1 of decoder_2_to_4_w_enable is

signal A0_n, A1_n: std_logic;
begin
A0_n <= not A0;
A1_n <= not A1;
D0 <= A0_n and A1_n and EN;
D1 <= A0 and A1_n and EN;
D2 <= A0_n and A1 and EN;
D3 <= A0 and A1 and EN;
end dataflow_1;
```

EN	A ₁	A ₀	D ₀	D ₁	D ₂	D ₃
0	X	X	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1

 

VHDL para Decodificador 2 x 4

Descrição Fluxo de Dados

-- 2-to-4 Line Decoder: Dataflow VHDL
Description

-- (See Figure 4-10 for logic diagram)

```
library ieee, lcdf_vhdl;  
use ieee.std_logic_1164.all,  
    lcdf_vhdl.func_prims.all;  
  
entity decoder_2_to_4_w_enable is  
    port(EN, A0, A1: in std_logic;  
         D0, D1, D2, D3: out std_logic);  
end decoder_2_to_4_w_enable;
```

architecture dataflow_1 of
decoder_2_to_4_w_enable is

```
    signal A0_n, A1_n: std_logic;  
begin  
    A0_n <= not A0;  
    A1_n <= not A1;  
    D0 <= A0_n and A1_n and EN;  
    D1 <= A0 and A1_n and EN;  
    D2 <= A0_n and A1 and EN;  
    D3 <= A0 and A1 and EN;  
end dataflow_1;
```

VHDL para Decodificador 2 x 4

Descrição Estrutural

```


• library ieee, lcdf_vhdl;
• use ieee.std_logic_1164.all, lcdf_vhdl.func_prims.all;
• entity decoder_2_to_4_w_enable is
•   port(EN, A0, A1: in std_logic;
•     D0, D1, D2, D3: out std_logic);
• end decoder_2_to_4_w_enable;

• architecture structural_1 of decoder_2_to_4_w_enable is
• component NOT1
•   port(in1: in std_logic;
•     out1: out std_logic);
• end component;
• component AND2
•   port(in1, in2: in std_logic;
•     out1: out std_logic);
• end component;
• signal A0_n, A1_n, N0, N1, N2, N3: std_logic;
• begin
•   g0: NOT1 port map (in1 => A0, out1 => A0_n);
•   g1: NOT1 port map (in1 => A1, out1 => A1_n);
•   g2: AND2 port map (in1 => A0_n, in2 => A1_n, out1 => N0);
•   g3: AND2 port map (in1 => A0, in2 => A1_n, out1 => N1);
•   g4: AND2 port map (in1 => A0_n, in2 => A1, out1 => N2);
•   g5: AND2 port map (in1 => A0, in2 => A1, out1 => N3);
•   g6: AND2 port map (in1 => EN, in2 => N0, out1 => D0);
•   g7: AND2 port map (in1 => EN, in2 => N1, out1 => D1);
•   g8: AND2 port map (in1 => EN, in2 => N2, out1 => D2);
•   g9: AND2 port map (in1 => EN, in2 => N3, out1 => D3);
• end structural_1;


```

-- 2-to-4 Line Decoder with Enable: Structural VHDL Description
 -- (See Figure 4-10 for logic diagram)

EN	A ₁	A ₀	D ₀	D ₁	D ₂	D ₃
0	X	X	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1

 

Visão de Conjunto

 

Test Bench para o MUX 4 x 1

```
library ieee;
use ieee.std_logic_1164.all;

entity TestBench_MUX4 is
end;

architecture BENCH of TestBench_MUX4 is
component MUX_4_to_1_WE
port (S :in std_logic_vector(1 downto 0);
      I :in std_logic_vector(0 to 3);
      Y :out std_logic);
end component;
signal S: std_logic_vector(1 downto 0);
signal I: std_logic_vector(0 to 3);

begin
  DUT: MUX_4_to_1_WE port map (S => S, I(0) => I(0), I(1) => I(1), I
(2) => I(2), I(3) => I(3));
  S <= "00", "01" after 30 NS, "10" after 60 NS,
"11" after 90 NS, "XX" after 120 NS,
"00" after 130 NS;
  I(0) <= 'X', '0' after 10 NS, '1' after 20 NS;
  I(1) <= 'X', '0' after 40 NS, '1' after 50 NS;
  I(2) <= 'X', '0' after 70 NS, '1' after 80 NS;
  I(3) <= 'X', '0' after 100 NS, '1' after 110 NS;
end BENCH;
```

Um *testbench* é usado para produzir os sinais de teste de um dispositivo modelado em VHDL

VHDL para Circuitos Sequenciais

Normalmente o corpo de um processo implementa um programa sequencial

No entanto, os valores atribuídos a **sinais** só mudam no final do processo

Considere as atribuições, com $A = 6$, $B = 9$ e $C = 4$:

$B \leq A;$

$C \leq B;$

No final do processo,
 $B = 6$ e $C = 9$!!!!!

Considere agora que A , B e C tivessem sido declarados com **variáveis**, então:

$B := A;$


$C := B;$

Como para variáveis os valores são transmitidos instantaneamente,
 $B = 6$ e $C = 6$!!!!!

Variáveis só aparecem dentro de processos !


Timing Model

 - VHDL uses the following simulation cycle to model the stimulus and response nature of digital hardware



Delay Types

 
- All VHDL signal assignment statements prescribe an amount of time that must transpire before the signal assumes its new value
- This prescribed delay can be in one of three forms:
 - Transport -- prescribes propagation delay only
 - Inertial -- prescribes propagation delay and minimum input pulse width
 - Delta -- the default if no delay time is explicitly specified



Transport Delay

- Transport delay must be explicitly specified
 - I.e. keyword “TRANSPORT” must be used
- Signal will assume its new value after specified delay
 
```
-- TRANSPORT delay example  
Output <= TRANSPORT NOT Input AFTER 10 ns;
```




Inertial Delay

- Provides for specification propagation delay and input pulse width, i.e. ‘inertia’ of output:

```
target <= [REJECT time_expression] INERTIAL waveform;
```

- Inertial delay is default and REJECT is optional :

 
```
Output <= NOT Input AFTER 10 ns;  
-- Propagation delay and minimum pulse width are 10ns
```



Inertial Delay (cont.)

 - Example of gate with 'inertia' smaller than propagation delay
 - e.g. Inverter with propagation delay of 10ns which suppresses pulses shorter than 5ns

Output <= REJECT 5ns INERTIAL NOT Input AFTER 10ns;



Delta Delay


- Default signal assignment propagation delay if no delay is explicitly prescribed
 - VHDL signal assignments do not take place immediately
 - Delta is an infinitesimal VHDL time unit so that all signal assignments can result in signals assuming their values at a future time
 - E.g.

```
Output <= NOT Input;  
-- Output assumes new value in one delta cycle
```
- Supports a model of concurrent VHDL process execution
 - Order in which processes are executed by simulator does not affect simulation output

Delta Delay

An Example without Delta Delay

- What is the behavior of C?

 

NAND gate evaluated first:

IN: 1->0

A: 0->1

B: 1->0

C: 0->0

AND gate evaluated first:

IN: 1->0

A: 0->1

C: 0->1


B: 1->0

C: 1->0

Delta Delay

An Example with Delta Delay

- What is the behavior of C?

 

Using delta delay scheduling

<u>Time</u>	<u>Delta</u>	<u>Event</u>
0 ns	1	IN: 1->0 eval INVERTER
	2	A: 0->1 eval NAND, AND
	3	B: 1->0 C: 0->1 eval AND
	4	C: 1->0
1 ns		

Signals and Variables

- This example highlights the difference between signals and variables

```
ARCHITECTURE test1 OF mux IS
    SIGNAL x : BIT := '1';
    SIGNAL y : BIT := '0';
BEGIN
    PROCESS (in_sig, x, y)
    BEGIN
        x <= in_sig XOR y;
        y <= in_sig XOR x;
    END PROCESS;
END test1;
```

```
ARCHITECTURE test2 OF mux IS
    SIGNAL y : BIT := '0';
BEGIN
    PROCESS (in_sig, y)
        VARIABLE x : BIT := '1';
    BEGIN
        x := in_sig XOR y;
        y <= in_sig XOR x;
    END PROCESS;
END test2;
```

- Assuming a 1 to 0 transition on *in_sig*, what are the resulting values for *y* in the both cases?

VHDL Objects

Signals vs Variables

- A key difference between variables and signals is the assignment delay

```
ARCHITECTURE sig_ex OF test IS
  PROCESS (a, b, c, out_1)
  BEGIN
    out_1 <= a NAND b;
    out_2 <= out_1 XOR c;
  END PROCESS;
END sig_ex;
```

Time	a	b	c	out_1	out_2
0	0	1	1	1	0
1	1	1	1	1	0
1+d	1	1	1	0	0
1+2d	1	1	1	0	1

VHDL Objects

Signals vs Variables (Cont.)

```
ARCHITECTURE var_ex OF test IS
BEGIN
    PROCESS (a, b, c)
    VARIABLE out_3 : BIT;
    BEGIN
        out_3 := a NAND b;
        out_4 <= out_3 XOR c;
    END PROCESS;
END var_ex;
```

Time	a	b	c	out_3	out_4
0	0	1	1	1	0
1	1	1	1	0	0
1+d	1	1	1	0	1

VHDL para FF tipo D Disparado por Borda de Subida

```
-- Positive Edge-Triggered D Flip-Flop with Reset:  
-- VHDL Process Description
```


```
library ieee;  
use ieee.std_logic_1164.all;  
  
entity dff is  
  port(CLK, RESET, D: in std_logic;  
        Q, Q_n: out std_logic);  
end dff;
```

Neste processo, “D” não aparece na lista de sensibilidade porque uma mudança no valor de “D” não pode iniciar uma mudança em “Q” !

```
architecture pet_pr of dff is  
  -- Implements positive edge-triggered bit state storage  
  -- with asynchronous reset.  
  signal state: std_logic;  
begin  
  Q <= state;  
  Q_n <= not state;  
  process (CLK, RESET)  
  begin  
    if (RESET = '1') then  
      state <= '0';  
    else  
      if (CLK'event and CLK = '1') then  
        state <= D;  
      end if;  
    end if;  
  end process;  
end;
```

Diagrama Lógico do Reconhecedor 1101

 Foram usados
FFs tipo D
com Reset
não-invertido



Descrição VHDL do Reconhecedor de Sequência (1101) – Estado Atual


```
-- Sequence Recognizer: VHD Process Description
-- (See Figure 6-24(d) for state diagram)
```

```
library ieee;
use ieee.std_logic_1164.all;
entity seq_rec is
    port(CLK, RESET, X: in std_logic;
         Z: out std_logic);
end seq_rec;
```

```
architecture process_3 of seq_rec is
    type state_type is (A, B, C, D);
    signal state, next_state : state_type;
begin
```


```
-- Process 1 - state_register: implements positive edge-triggered
-- state storage with asynchronous reset.
```
 
```
state_register: process (CLK, RESET)
begin
    if (RESET = '1') then
        state <= A;
    elsif (CLK'event and CLK = '1') then
        state <= next_state;
    end if;
end if;
end process;
```



Descrição VHDL do Reconhecedor de Sequência (1101) – Próximo Estado

```
-- Process 2 - next_state_function: implements next state as
-- a function of input X and state.
next_state_func: process (X, state)
begin
  case state is
    when A =>
      if X = '1' then
        next_state <= B;
      else
        next_state <= A;
      end if;
    when B =>
      if X = '1' then
        next_state <= C;
      else
        next_state <= A;
      end if;
    when C =>
      if X = '1' then
        next_state <= C;
      else
        next_state <= D;
      end if;
    when D =>
      if X = '1' then
        next_state <= B;
      else
        next_state <= A;
      end if;
    end cas;
  end process;
```

 

Descrição VHDL do Reconhecedor de Sequência (1101) – Saída

```
-- Process 3 - output_function: implements output as function
-- of input X and state.
output_func: process (X, state)
begin
    case state is
        when A =>
            Z <= '0';
    when B =>
            Z <= '0';
    when C =>
            Z <= '0';
        when D =>
            if X = '1' then
                Z <= '1';
            else
                Z <= '0';
            end if;
        end case;
    end process;
end;
```

